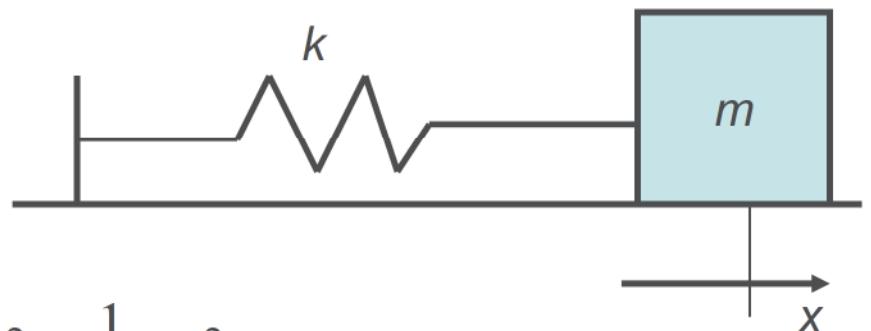


Example of Linear Spring Mass System and Frictionless Table: **The Steps**




$$\text{Lagrangian : } L = K_e - V = \frac{1}{2} m \dot{x}^2 - \frac{1}{2} k x^2$$

$$\text{Lagrang's Equation : } \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{q}_i} \right) - \frac{\partial L}{\partial q_i} = 0$$

$$\text{Do the derivatives : } \frac{\partial L}{\partial \dot{q}_i} = m \dot{x}; \quad \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{q}_i} \right) = m \ddot{x}; \quad \frac{\partial L}{\partial q_i} = -k x$$

$$\text{Combine all together : } \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{q}_i} \right) - \frac{\partial L}{\partial q_i} = m \ddot{x} + kx = 0$$

Mechanical Example: Mass-Spring Damper

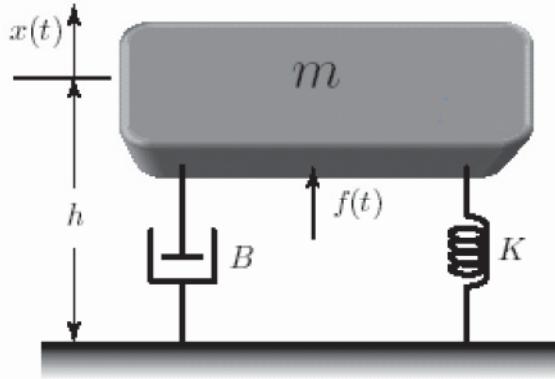

$$K_e = \frac{1}{2}m\dot{x}^2$$

$$V = \frac{1}{2}Kx^2 + mg(h+x)$$


$$L = K_e - V = \frac{1}{2}m\dot{x}^2 - \frac{1}{2}Kx^2 - mg(h+x)$$

$$P = \frac{1}{2}B\dot{x}^2$$

We have the generalized coordinate $q = x$, and thus with the applied force $Q = f$, we write the Lagrange equation :

$$\begin{aligned} f &= \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{x}} \right) - \frac{\partial L}{\partial x} + \frac{\partial P}{\partial \dot{x}} \\ &= \frac{d}{dt} \left(\frac{\partial}{\partial \dot{x}} \left(\frac{1}{2}m\dot{x}^2 - \frac{1}{2}Kx^2 - mg(h+x) \right) \right) \\ &\quad - \frac{\partial}{\partial x} \left(\frac{1}{2}m\dot{x}^2 - \frac{1}{2}Kx^2 - mg(h+x) \right) + \frac{\partial}{\partial \dot{x}} \left(\frac{1}{2}B\dot{x}^2 \right) \\ &= \frac{d}{dt} (m\dot{x}^2) - (-Kx - mg) + (B\dot{x}) \\ &= m\ddot{x} + Kx + mg + B\dot{x} \end{aligned}$$

Electrical Example: RLC Circuit

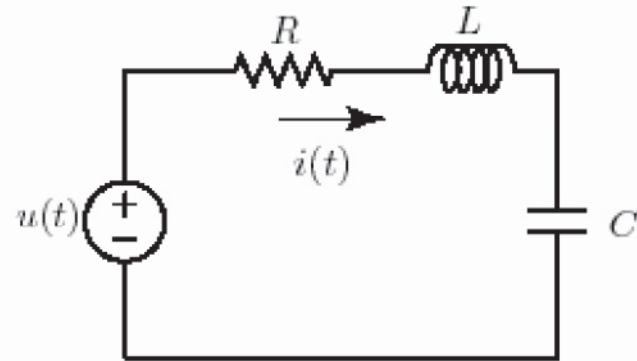

$$K_e = \frac{1}{2} L \dot{q}^2$$

$$V = \frac{1}{2C} q^2$$

$$L = K_e - V = \frac{1}{2} L \dot{q}^2 - \frac{1}{2C} q^2$$

$$P = \frac{1}{2} R \dot{q}^2$$


We have the generalized coordinate q (charge), and with the applied force $Q = u$, we have

$$\begin{aligned} u &= \frac{d}{dt} \left(\frac{\partial L}{\partial \dot{q}} \right) - \frac{\partial L}{\partial q} + \frac{\partial P}{\partial \dot{q}} \\ &= \frac{d}{dt} \left(\frac{\partial}{\partial \dot{q}} \left(\frac{1}{2} L \dot{q}^2 - \frac{1}{2C} q^2 \right) \right) - \frac{\partial}{\partial q} \left(\frac{1}{2} L \dot{q}^2 - \frac{1}{2C} q^2 \right) + \frac{\partial}{\partial \dot{q}} \left(\frac{1}{2} R \dot{q}^2 \right) \\ &= \frac{d}{dt} (L \dot{q}) + \frac{Q}{C} + R \dot{q} = L \ddot{q} + \frac{Q}{C} + R \dot{q} = L \frac{di}{dt} + v_c + Ri \end{aligned}$$

$i = \dot{q}$ and $q = Cv_c$ for a capacitor. This is just KVL equation

Electromechanical System: Capacitor Microphone

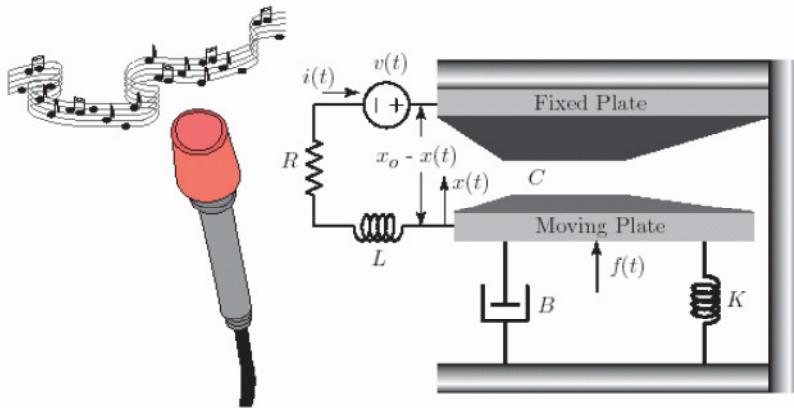About them see: <http://www.soundonsound.com/sos/feb98/articles/capacitor.html>



This system has two degrees of freedom (electrical and mechanical: charge q and displacement x from equilibrium)

$$K_e = \frac{1}{2} L \dot{q}^2 + \frac{1}{2} m \dot{x}^2; V = \frac{1}{2C} q^2 + \frac{1}{2} K x^2$$

$$C = \frac{\epsilon A}{x_o - x} \left(\begin{array}{l} \epsilon \text{ is the dielectric constant of the air (F/m),} \\ A \text{ is the area of the plate, } x_o - x \text{ is the plate separation} \end{array} \right)$$

$$V = \frac{1}{2 \epsilon A} (x_o - x) q^2 + \frac{1}{2} K x^2; P = \frac{1}{2} R \dot{q}^2 + \frac{1}{2} B \dot{x}^2$$

$$L = \frac{1}{2} L \dot{q}^2 + \frac{1}{2} m \dot{x}^2 - \frac{1}{2 \epsilon A} (x_o - x) q^2 - \frac{1}{2} K x^2$$

$$\frac{\partial L}{\partial \dot{x}} = m\dot{x}; \quad \frac{\partial L}{\partial x} = \frac{q^2}{2\varepsilon A} - Kx; \quad \frac{\partial P}{\partial \dot{x}} = B\dot{x}$$


$$\frac{\partial L}{\partial \dot{q}} = L\dot{q}; \quad \frac{\partial L}{\partial q} = \frac{(x_o - x)q}{\varepsilon A}; \quad \frac{\partial P}{\partial \dot{q}} = R\dot{q}$$

Then we obtain the two Lagrange equations

$$m\ddot{x} + B\dot{x} + Kx - \frac{q^2}{2\varepsilon A} = f$$

$$L\ddot{q} + R\dot{q} + \frac{1}{\varepsilon A}(x_o - x)q = v$$

Example: Two Mesh Electric Circuit

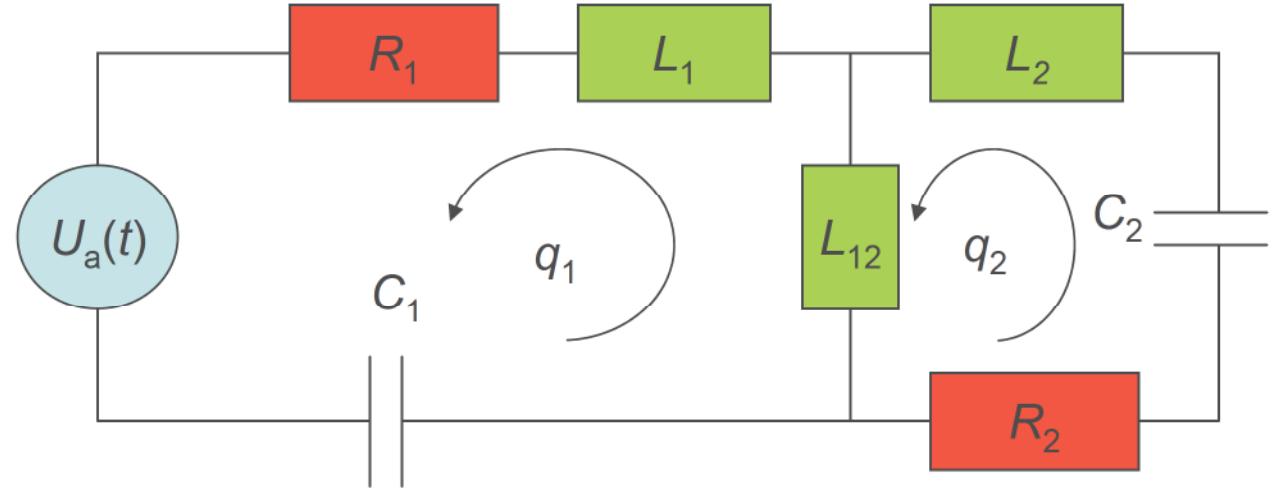

Assume q_1 and q_2 as the independent generalized coordinates, where q_1 is the electric charge in the first loop and q_2 is the electric charge in the second loop.

The generalized force applied to the system is denoted as Q_1

We should know that : $i_1 = \dot{q}_1$; $i_2 = \dot{q}_2$; $q_1 = \frac{i_1}{s}$; $q_2 = \frac{i_2}{s}$; $Q_1 = U_a(t)$.

The total magnetic energy (kinetic energy) is :

$$K_e = \frac{1}{2} L_1 \dot{q}_1^2 + \frac{1}{2} L_{12} (\dot{q}_1 - \dot{q}_2)^2 + \frac{1}{2} L_2 \dot{q}_2^2$$

$$\frac{\partial K_e}{\partial q_1} = 0; \quad \frac{\partial K_e}{\partial \dot{q}_1} = (L_1 + L_{12})\dot{q}_1 - L_{12}\dot{q}_2$$

$$\frac{\partial K_e}{\partial q_2} = 0; \quad \frac{\partial K_e}{\partial \dot{q}_2} = (L_2 + L_{12})\dot{q}_2 - L_{12}\dot{q}_1$$

Use the equation for the total electric energy (potential energy)

$$V = \frac{1}{2} \frac{q_1^2}{C_1} + \frac{1}{2} \frac{q_2^2}{C_2}; \quad \frac{\partial V}{\partial q_1} = \frac{q_1}{C_1} \quad \text{and} \quad \frac{\partial V}{\partial q_2} = \frac{q_2}{C_2}$$


The total heat energy dissipated: $P = \frac{1}{2} R_1 \dot{q}_1^2 + \frac{1}{2} R_2 \dot{q}_2^2; \quad \frac{\partial P}{\partial \dot{q}_1} = R_1 \dot{q}_1 \quad \text{and} \quad \frac{\partial P}{\partial \dot{q}_2} = R_2 \dot{q}_2$

$$\frac{d}{dt} \left(\frac{\partial K_e}{\partial \dot{q}_1} \right) - \frac{\partial K_e}{\partial q_1} + \frac{\partial P}{\partial \dot{q}_1} + \frac{\partial V}{\partial q_1} = Q_1; \quad \frac{d}{dt} \left(\frac{\partial K_e}{\partial \dot{q}_2} \right) - \frac{\partial K_e}{\partial q_2} + \frac{\partial P}{\partial \dot{q}_2} + \frac{\partial V}{\partial q_2} = 0$$

$$(L_1 + L_{12})\ddot{q}_1 - L_{12}\ddot{q}_2 + R_1 \dot{q}_1 + \frac{q_1}{C_1} = U_a; \quad -L_{12}\ddot{q}_1 + (L_2 + L_{12})\ddot{q}_2 + R_2 \dot{q}_2 + \frac{q_2}{C_2} = 0$$

$$\ddot{q}_1 = \frac{1}{(L_1 + L_{12})} \left(-\frac{q_1}{C_1} - R_1 \dot{q}_1 + L_{12}\ddot{q}_2 + U_a \right); \quad \ddot{q}_2 = \frac{1}{(L_2 + L_{12})} \left(L_{12}\ddot{q}_1 - \frac{q_2}{C_2} - R_2 \dot{q}_2 \right)$$

Another Example

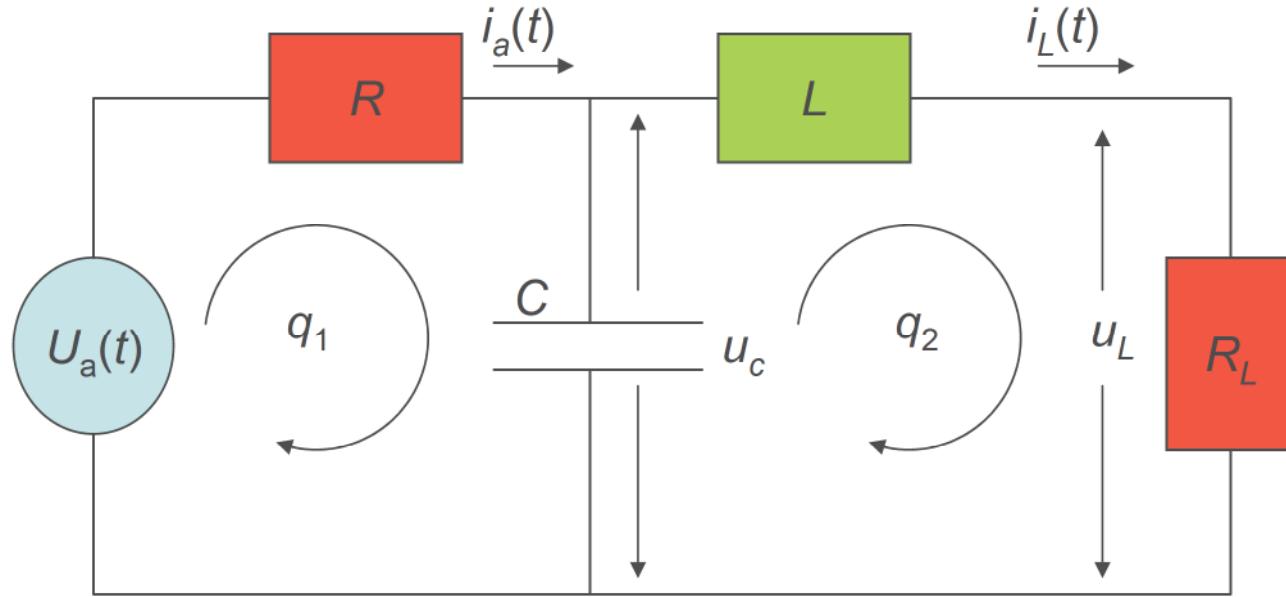

Use q_1 and q_2 as the independent generalized coordinates :

$$i_a = \dot{q}_1; i_L = \dot{q}_2; u_a(t) = Q_1$$

$$K_e = \frac{1}{2} L \dot{q}_2^2; \quad \frac{\partial K_e}{\partial q_1} = 0; \quad \frac{\partial K_e}{\partial \dot{q}_1} = 0; \quad \frac{d}{dt} \left(\frac{\partial K_e}{\partial \dot{q}_1} \right) = 0$$

$$\frac{\partial K_e}{\partial q_2} = 0; \quad \frac{\partial K_e}{\partial \dot{q}_2} = L \dot{q}_2; \quad \frac{d}{dt} \left(\frac{\partial K_e}{\partial \dot{q}_2} \right) = L \ddot{q}_2$$

The total potential energy is : $V = \frac{1}{2} \frac{(q_1 - q_2)^2}{C}$

$$\frac{\partial V}{\partial q_1} = \frac{q_1 - q_2}{C} \quad \text{and} \quad \frac{\partial V}{\partial q_2} = \frac{-q_1 + q_2}{C}$$

The total dissipated energy is : $P = \frac{1}{2} R \dot{q}_1^2 + \frac{1}{2} R_L \dot{q}_2^2$

$$\frac{\partial P}{\partial \dot{q}_1} = R \dot{q}_1 \quad \text{and} \quad \frac{\partial P}{\partial \dot{q}_2} = R_L \dot{q}_2$$

$$\frac{d}{dt} \left(\frac{\partial K_e}{\partial \dot{q}_1} \right) - \frac{\partial K_e}{\partial q_1} + \frac{\partial P}{\partial \dot{q}_1} + \frac{\partial V}{\partial q_1} = Q_1; \quad \frac{d}{dt} \left(\frac{\partial K_e}{\partial \dot{q}_2} \right) - \frac{\partial K_e}{\partial q_2} + \frac{\partial P}{\partial \dot{q}_2} + \frac{\partial V}{\partial q_2} = 0$$

$$R \dot{q}_1 + \frac{q_1 - q_2}{C} = u_a; \quad L \ddot{q}_2 + R_L \dot{q}_2 + \frac{-q_1 + q_2}{C} = 0$$

$$\dot{q}_1 = \frac{1}{R} \left(\frac{-q_1 + q_2}{C} + u_a \right); \quad \ddot{q}_2 = \frac{1}{L} \left(-R_L \dot{q}_2 + \frac{q_1 - q_2}{C} \right)$$

By using Kirchhoff's law, we get

$$\frac{du_c}{dt} = \frac{1}{C} \left(-\frac{u_c}{R} - i_L + \frac{u_a(t)}{R} \right); \quad \frac{di_L}{dt} = \frac{1}{L} (u_c - R_L i_L)$$